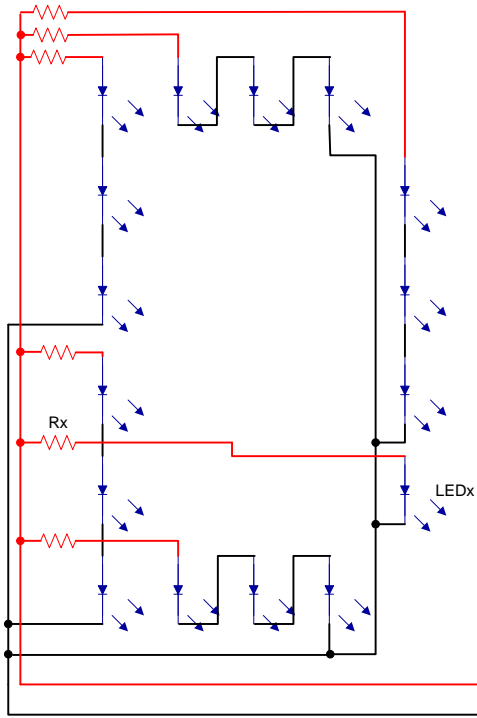


LED Matrix Character Display

<http://picprojects.org>

Design A


- Uses different value resistors depending on how many LEDs are in series.
- Uses less current since most LEDs are in series.
- Needs a power supply voltage greater than the sum of the forward voltages of the LEDs connected in series.



Note:
Since current limit resistor Rx connects to only one LED it needs to be a different value from the other resistors that connect to three LEDs



Design B

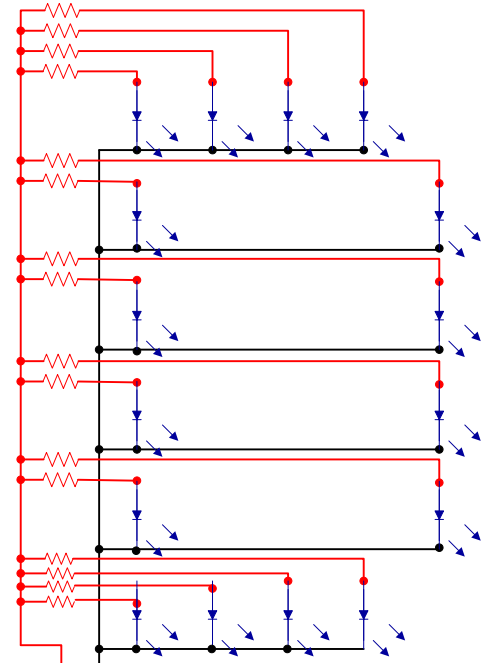- Use same value resistor for all LEDs
- Requires more current since all LEDs are in parallel



Arrange LEDs in a 5 x 7 matrix

For letter I or digit 1, use 3 x 7

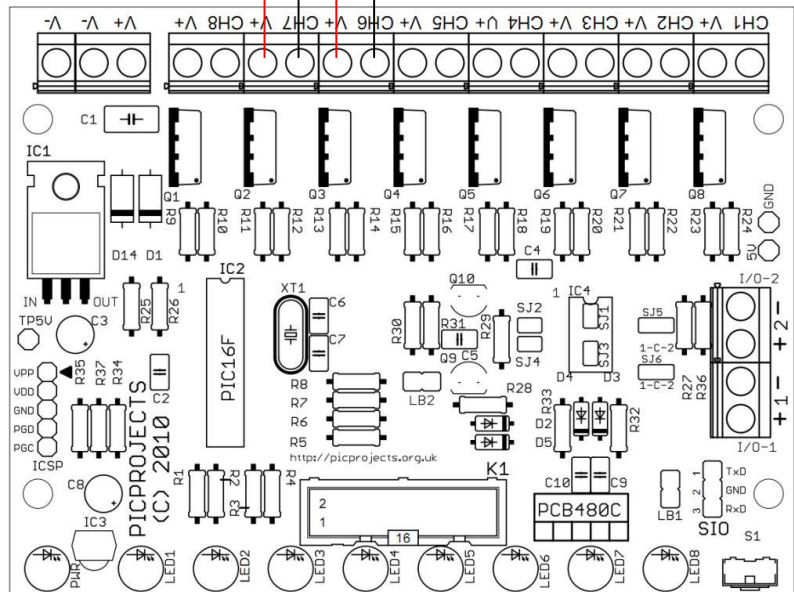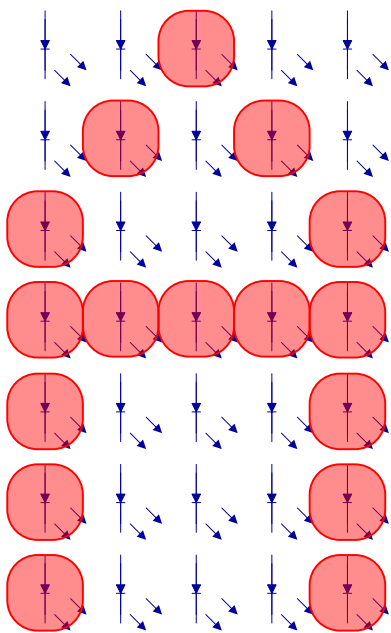

- For calculating the LED current limit resistors required see <http://picprojects.org.uk/projects/inf/drivingLEDs.pdf>
- Make sure the power supply used can deliver the required current to power all the LEDs attached to the controller
- For details of the controller PCB shown see <http://picprojects.org.uk/projects/480/pro483/>