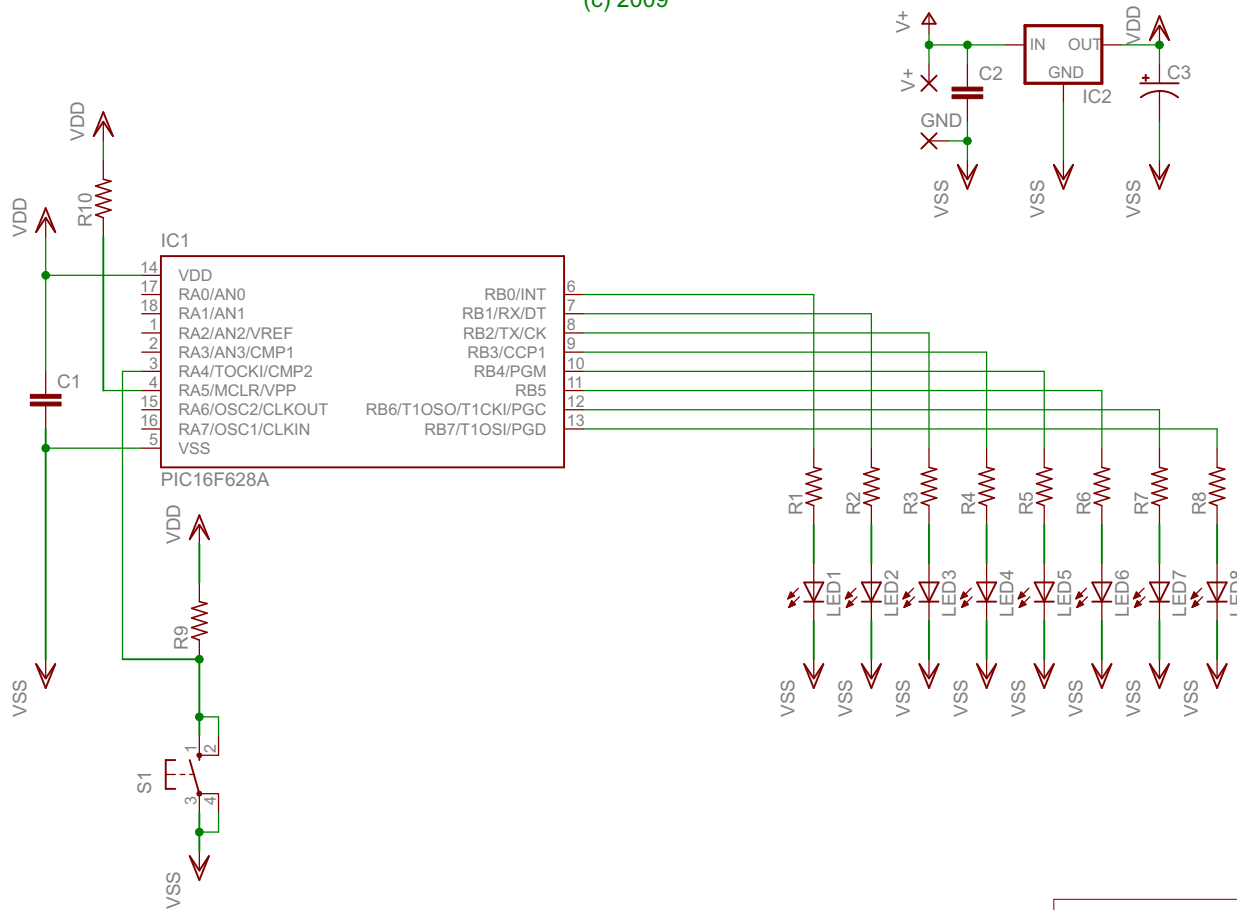


Round PWM LED Chaser

<http://picprojects.org.uk>

(c) 2009



R1-R8 330R
R9, R10 10K

C1 100nF disc ceramic
C2 100nF disc ceramic
C3 47uF / 6.3V

IC1 PIC 16F628A

IC2 LM2931-5.0, 100mA 5v LDO regulator
LED1-8 5mm RED high brightness

S1 Omron B3F-31XX or similar

Resistors 5% 1/4 or 1/8 watt carbon film