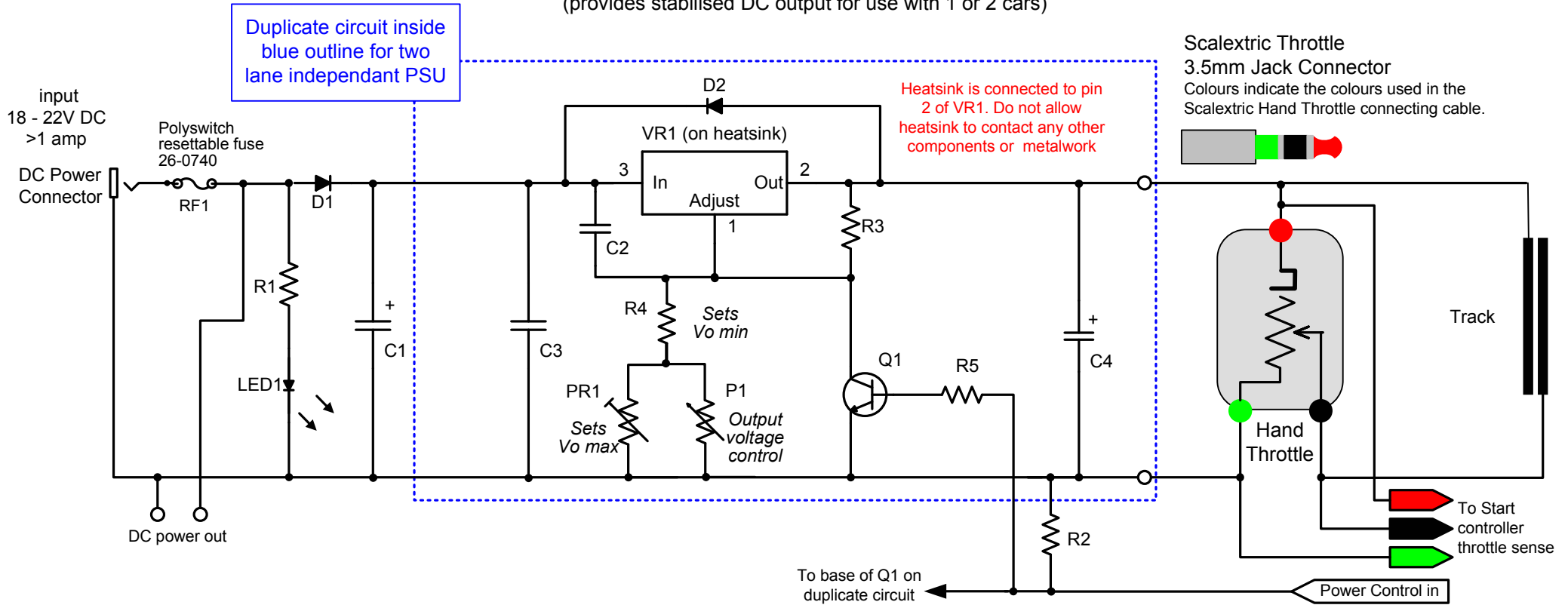


Variable voltage DC power supply with
track power shutdown for Scalextric 1/32 slot car track.
(provides stabilised DC output for use with 1 or 2 cars)



Power Supply Notes

Do not use the original Scalextric PSU as this outputs AC not DC. The Powerbase rectifies the AC to DC but does not smooth the supply so should also not be used.

Suitable PSU for input to this circuit should deliver 18-22V DC at 1 Amp or greater. Any PSU meeting this requirement can be used. For example 18V/1.1A supply from Rapid Electronics P/N PW00752.

This circuit is for use with standard Scalextric cars using stock electric motors.

Component List

Resistors

- R1 0.25watt 5%
- R2 47K Ω
- R3 220 Ω
- R4 1K Ω
- R5 3.3K Ω
- PR1 2K Ω enclosed preset (Rapid Electronics P/ N 68-0045)
- P1 4.7K Ω linear potentiometer (Rapid Electronics P/ N 65-0710)

Capactors

- C1 2200 μ F / 35volt electrolytic
- C2, C3 100nF ceramic
- C4 10 μ F / 25volt Tantalum

Semiconductor

- VR1 LM317T 3-terminal adjustable regulator 1.5 amp
- D1 1N5401
- D2 1N4001
- LED1 Green 5mm
- Q1 BC548 npn transistor
- RF1 1.1A Polyswitch resettable fuse (Rapid Electronics P/N 26-0740)

Hardware

- Heatsink for IC1 3.9 $^{\circ}$ C/W (Rapid Electronics P/N 36-0316 or similar)
- M3 6mm screw and M3 nut to fix VR1 to heatsink
- Knob to fit voltage adjust potentiometer P1
- 2.1mm or 2.5mm DC Power connector to suit DC power supply

Componet List

For the second track PSU, duplicate all components appended with an 'a' on the schematic / component list.

Resistors

	0.25watt 5%
R1	1.5K Ω
R2a	1K Ω
R3a	220 Ω
R4,5,6,7,8	270 Ω
R9,10	10K Ω
R12a	470 Ω 0.5watt

Capactiors

C1a	470 μ F / 35volt electrolytic
C2a	100nF polyester
C3a	22 μ F / 35volt electrolytic
C4	100nF polyester
C5	330nF polyester

Potentiometers

P1a	5K Ω enclosed preset
P2a	2.2K Ω linear potentiometer

Semiconductor

IC1a	LM317T 3-terminal adjustable regulator 1.5 amp
IC2	LM7805 5V regulator, 1 amp
IC3	PIC 16F627A (programmed with start controller code)
IC4a	CNY17-4 opto coupler
D1a	1N5401
D2a	1N4001
D3a	1N4148 or 1N914
LED1	Green 5mm
LED2,3,4,5,6	Red 5mm high efficiency LED
Q1, Q2	BC548 npn transistor

Switches


SW1	SPST toggle switch
SW2	momentary on, push button

Hardware

Heatsink for IC1a	3.9 $^{\circ}$ C/W (Rapid Electronics P/N 36-0316 or similar)
Knob to fit voltage adjust potentiometer P2a	(x 2 if dual output)
2.1mm or 2.5mm DC Power connector	to suit DC power supply

Slot Car Race Start Controller

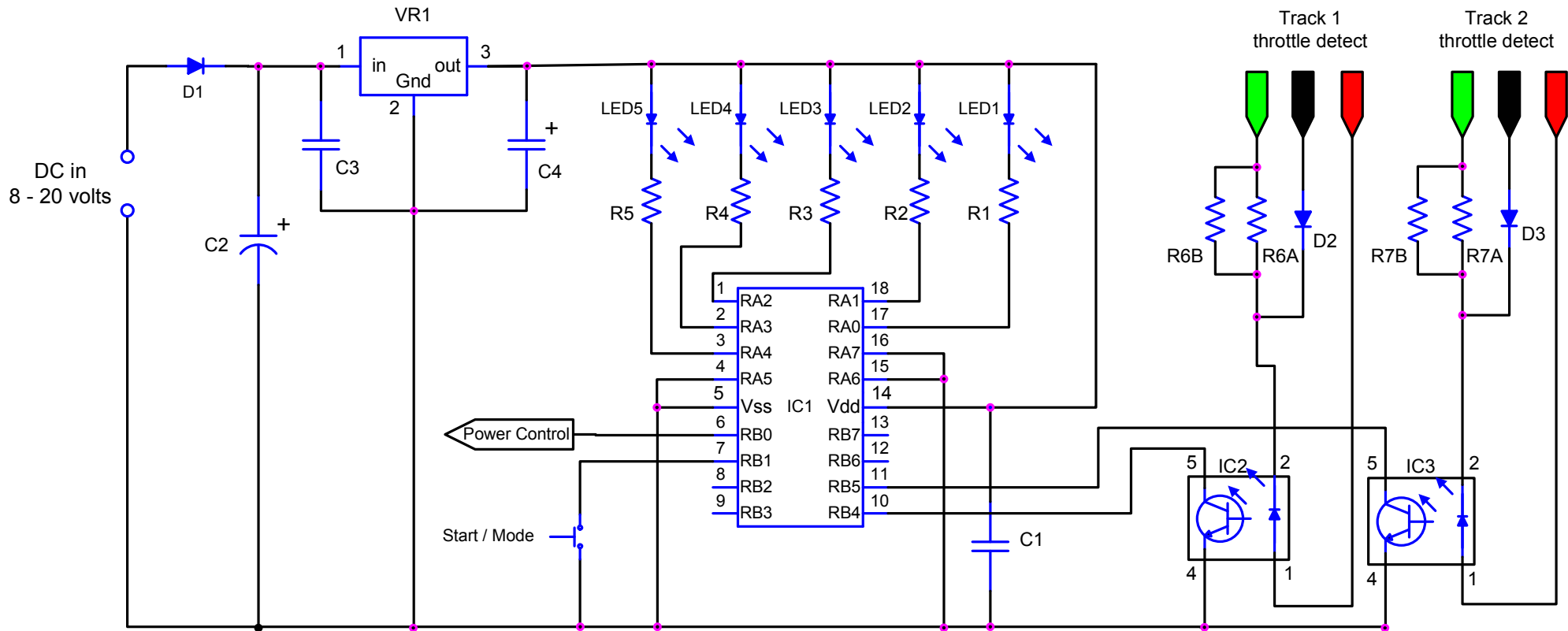with Jump Start Detection and Track Power Control
(for positive common rail throttles supplied with Scalextric Sport Track)



Componet List

Resistors

R1-5 0.25watt 5%
R1-5 220Ω
R6A,B 1.2KΩ
R7A,B 1.2KΩ
See Important Note (right)

Capactors

C1 47nF ceramic
C2 220μF / 35volt electrolytic
C3 100nF ceramic
C4 10μF / 10 volt tantalum

Semiconductor

VR1 LM7805 5V regulator, 1 amp
IC1 PIC 16F627A (programmed with start controller code)
IC2,3 CNY17-4 opto coupler
D1 1N4001
D2,3 1N4148 or 1N914
LED1,2,3,4,5 Red 5mm high efficiency LED

Switch

SW1 momentary on, push button

Important Note:

When used with the Scalextric Sport Powerbase and original transformer, omit R6B / R7B and use 1.8KΩ 0.25watt resistors for R6A / R7A.